

Soln. 1(a.) :

Phevenin's equivalent circuit

Calculation of V_{th} :

from loop (1) ;

$$I = \frac{4 - \frac{V_{ab}}{1000}}{8k} \quad \text{--- (1)}$$

from outer loop;

$$V_{th} = -8I \times 50k \quad (\because V_{th} = V_{ab})$$

$$V_{th} = -400 I \text{ K } V$$

from Eqⁿ(1);



$$V_{th} = -\frac{400}{8k} \left(4 - \frac{V_{th}}{1000} \right) \text{ K}$$

$$V_{th} = \frac{400 V_{th}}{8000} - \frac{16 \text{ mV}}{8} = \frac{V_{th}}{20} - 2 \text{ mV}$$

$$\frac{19 V_{th}}{20} = -2 \text{ mV}$$


$$V_{th} = \frac{-2 \text{ mV} \times 20}{19} = -210.52 \text{ mV}$$

$V_{th} = -210.52 \text{ Volt}$

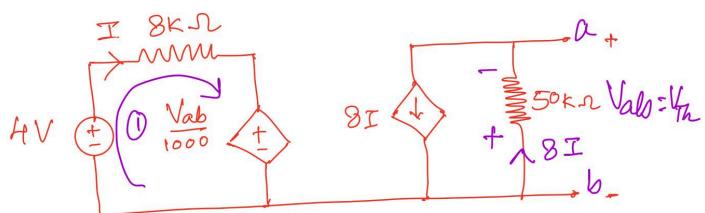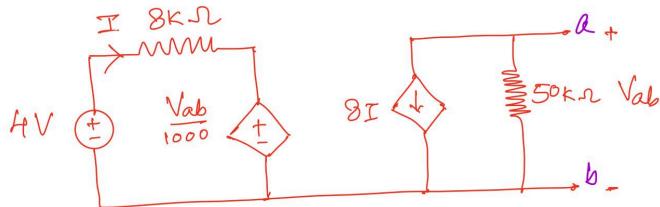Calculation of R_{th} :A volt source \rightarrow short circuited

from loop (1) ;

$$I = -\frac{V_{ab}/1000}{8k}$$

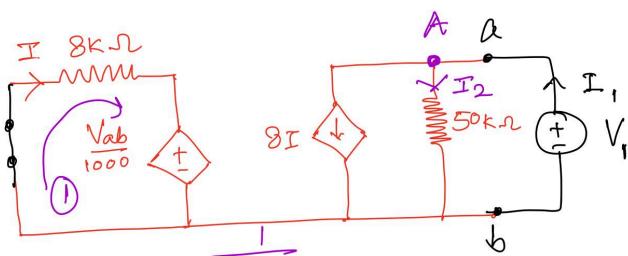

$$I = -\frac{V_r}{8000k} \longrightarrow (1) \quad (\because V_{ab} = V_r)$$

Apply KCL at node A;

$$8I + I_2 - I_1 = 0$$

$$-\frac{8V_r}{8000k} + \frac{V_r}{50k} = I_1$$

$$V_r \left[\frac{1}{50k} - \frac{1}{1000k} \right] = I_1$$

$$R_{Th} = \frac{V_r}{I_1} = \frac{\frac{1}{20 - 1}}{\frac{1}{1000k}} = \frac{1000k}{19}$$

$$R_{Th} = 52.631 \text{ k}\Omega$$


Thevenin's Equivalent Circuit:

Condition for MPT:

$$R_L = R_{Th} = 52.631 \text{ k}\Omega$$

$$P_{max} = \frac{V_{Th}^2}{4R_L} = \frac{V_{Th}^2}{4R_{Th}} = \frac{(-210.52)^2}{4 \times 52.631 \text{ k}} = 210.51 \text{ mW}$$

$$P_{max} = 210.51 \text{ mW}$$

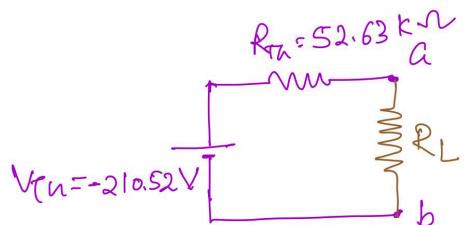


Soln 1. [b]:

Data Given:


$$\frac{V_o}{V_g} = 0.25$$
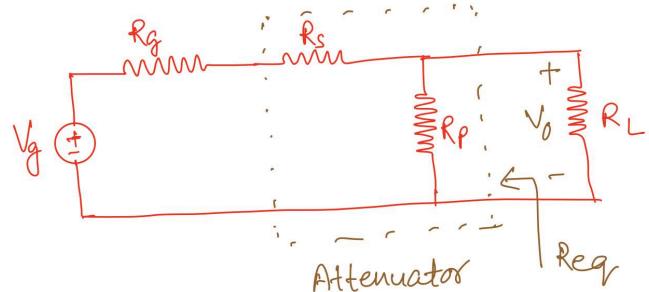
$$R_{eq} = R_g = R_{th} = 2 \text{ k}\Omega$$



$$R_{eq} = R_p \parallel (R_g + R_s) = R_g$$
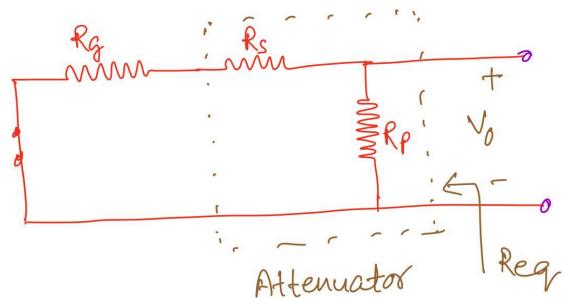
$$\frac{R_p \times (R_g + R_s)}{R_p + R_g + R_s} = R_g$$




$$R_p R_g + R_p R_s = R_p R_g + R_g^2 + R_g R_s$$

$$R_p R_s = R_g (R_g + R_s) \quad \text{--- (1)}$$

$$V_o = V_g \times \frac{R_p}{R_p + R_g + R_s}$$
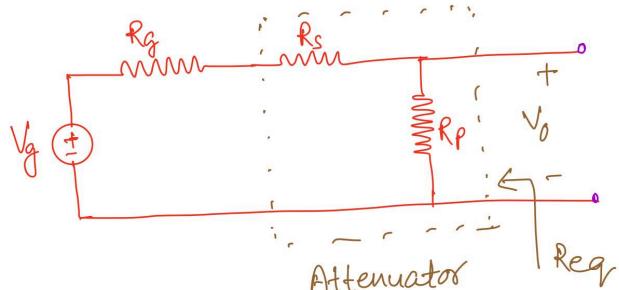
$$\frac{V_o}{V_g} = \frac{R_p}{R_p + R_g + R_s} = 0.25 = \frac{1}{4}$$



$$4 R_p = R_p + R_g + R_s$$

$$3 R_p = R_g + R_s \quad \text{--- (2)}$$

from eqn (1) & (2):

$$R_p R_s = R_g \times 3 R_p$$

$$R_s = 2 \times 3 \text{ k}\Omega = 6 \text{ k}\Omega$$


$$R_s = 6 \text{ k}\Omega$$

$$R_p = \frac{R_g + R_s}{3} = \frac{2k + 6k}{3} = \frac{8}{3} k\Omega$$

$$R_p = 2.67 k\Omega$$

Soln. 2[a]:

i_o, v_o using superposition principle

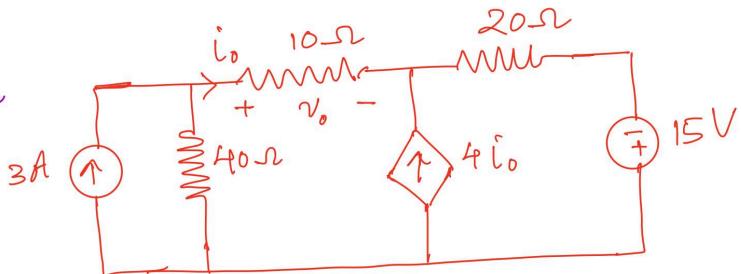

Case 1: 3A is Activated;
15V deactivated \equiv s/c

Using Nodal Analysis;


KCL at V_1 :

$$-3 + \frac{V_1}{40} + \frac{V_1 - V_2}{10} = 0$$

$$-120 + V_1 + 4V_1 - 4V_2 = 0$$

$$5V_1 - 4V_2 = 120 \quad \text{--- (1)}$$

$$i_o' = \frac{V_1 - V_2}{10}$$

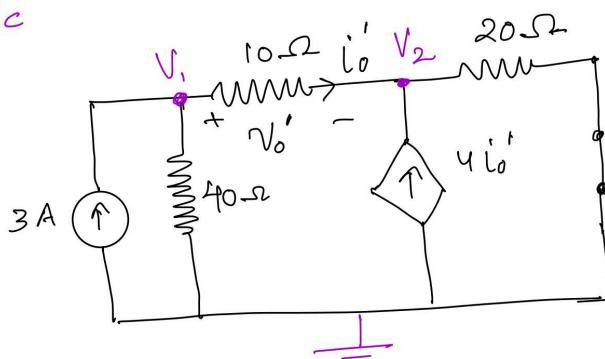

KCL at V_2 :

$$\frac{V_2 - V_1}{10} + \frac{V_2}{20} - 4i_o' = 0 \quad \text{--- (2)}$$

$$\frac{V_2 - V_1}{10} + \frac{V_2}{20} - \frac{4(V_1 - V_2)}{10} = 0$$

$$2V_2 - 2V_1 + V_2 - 8V_1 + 8V_2 = 0$$

$$10V_1 - 11V_2 = 0$$

$$V_1 = 1.1V_2 \quad \text{--- (3)}$$

From eqns (1) & (3),

$$5(1.1V_2) - 4V_2 = 120$$

$$5.5V_2 - 4V_2 = 120$$

$$1.5V_2 = 120$$

$$V_2 = \frac{120}{1.5} = \frac{400}{5} = 80 \text{ V}$$

$$V_2 = 80 \text{ V}$$

$$V_1 = 88 \text{ V}$$


$$i_o'' = \frac{V_1 - V_2}{10} = \frac{88 - 80}{10} = 0.8 \text{ A}$$

$$i_o' = 0.8 \text{ A}$$

$$V_o' = V_1 - V_2 = 8 \text{ V}$$

Case 2: Using Nodal Analysis,
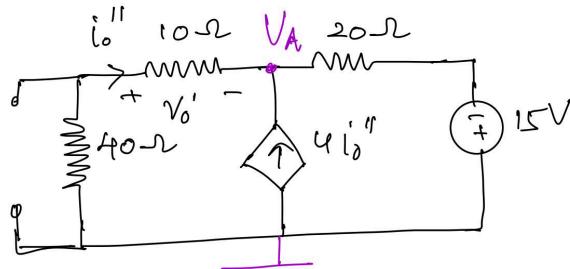
$$\frac{V_A}{50} + \frac{V_A - (-15)}{20} - 4i_o''' = 0$$



$$i_o''' = -\frac{V_A}{50}$$

$$-i_o''' + \frac{15 - 50i_o'''}{20} - 4i_o''' = 0$$

$$100i_o''' = 15 - 50i_o'''$$

$$i_o''' = \frac{15}{150} = \frac{1}{10} = 0.1 \text{ A}$$

$$i_o''' = 0.1 \text{ A}$$

$$V_o''' = 10 \times i_o''' = 1 \text{ V}$$

Using Superposition principle;

$$V_o = V_{oI} + V_{oII} = 8 + 1 = 9V$$

$$\boxed{V_o = 9V}$$

$$i_o = i_{oI} + i_{oII} = 0.8 + 0.1 = 0.9A$$

$$\boxed{i_o = 0.9A}$$

Soln 2[b]:

Calculation of I_N :

Apply KVL in loop ①;

$$-V_o - 20(-i_o - I_N) - 4V_o = 0$$

$$5V_o + 20i_o + 20I_N = 0 \quad \text{--- (1)}$$

$$V_o = 5(0.2i_o - I_N) \quad \text{--- (2)}$$

from eqn (1) & (2);

$$25(0.2i_o - I_N) + 20i_o + 20I_N = 0$$

$$5i_o - 25I_N + 20i_o + 20I_N = 0$$

$$25i_o - 5I_N = 0$$

$$5i_o = I_N \quad \text{--- (3)}$$

Apply KVL in loop (2);

$$-20(-0.8i_o - I_N) - 4V_o + 10i_o = 0$$


$$16i_o + 20I_N - 4V_o + 10i_o = 0$$

$$26i_o + 20I_N - 20(0.2i_o - I_N) = 0$$

$$26i_o - 4i_o + 20I_N + 20I_N = 0$$

$$22i_o + 40I_N = 0$$

$$11i_o + 20I_N = 0$$

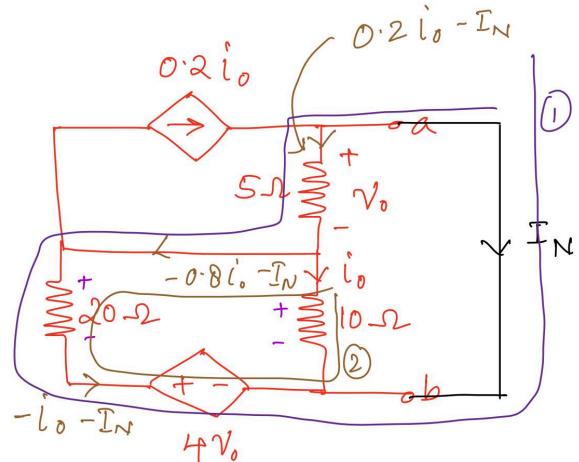

$$11i_o + 100i_o = 0$$

$$i_o = 0$$

$$I_N = 0 \text{ A}$$

Calculation of R_N :

Apply KVL in loop (1):

$$\nabla - 5(0.2i_o + I) - 20(-i_o + I)$$

$$-4 \times 5(0.2i_o + I) = 0$$

$$\nabla - i_o - 5I + 20i_o - 20I$$

$$-4i_o - 20I = 0$$

$$\nabla + 15i_o - 45I = 0 \quad \text{--- (1)}$$

Apply KVL in loop (2):

$$-20(-i_o + I) - 4 \times 5(0.2i_o + I) + 10i_o = 0$$

$$20i_o - 20I - 4i_o - 20I + 10i_o = 0$$

$$26i_o = 40I$$



$$i_o = \frac{40}{26}I \quad \text{--- (2)}$$

From Eq (1) & (2):

$$\nabla + 15 \times \frac{40}{26}I - 45I = 0$$

$$\frac{\nabla}{I} = 45 - \frac{600}{26} = \frac{570}{26}$$

$$\frac{\nabla}{I} = \frac{285}{13}$$

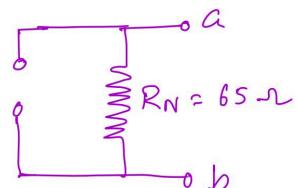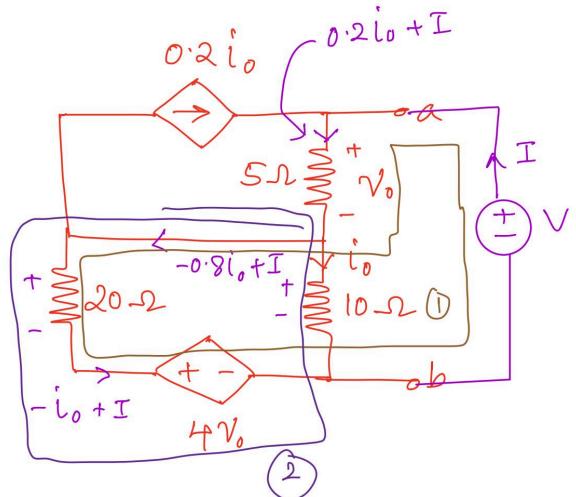

Norton's Equivalent Circuit

$$R_N = \frac{V}{I} = 21.92 \Omega$$

Soln 3 [a] :

Data Given:

$$V(0) = 0$$




for $0 < t < 1$

at $t = 0^+$

$$V(0^+) = V(0^-) = V(0) = 0 \text{ V}$$

at $t \rightarrow \infty$


$$V(\infty) = 2 \times 2 = 4 \text{ V}$$

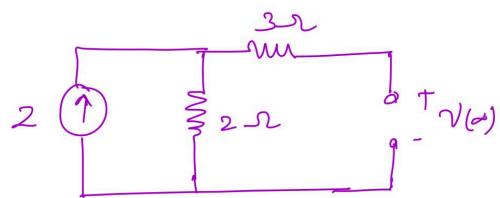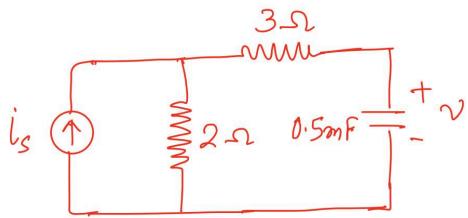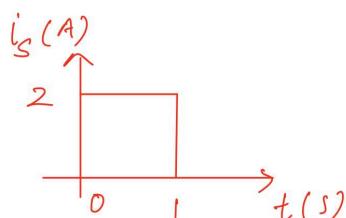

time constant $\tau = R_{eq} C$

$$R_{eq} = 3 + 2 = 5 \Omega$$
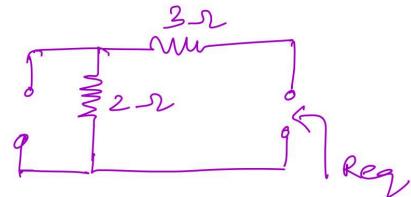
$$\tau = 5 \times 0.5 \text{ m} = 2.5 \text{ ms}$$



Voltage across capacitor ;

$$V(t) = V(\infty) + [V(0^-) - V(\infty)] e^{-t/\tau}$$

$$V(t) = 4 + (0 - 4) e^{-t/2.5 \text{ m}}$$

$$V(t) = 4(1 - e^{-400t}) \text{ volt}$$

for $t > 1$

at $t = 1^+$

$$V(1^+) = V(1^-) = V(1) = 4(1 - e^{-400}) = 4 \text{ V}$$


$$V(\infty) = 0$$

$$\tau = R_{eq} C = 5 \times 0.5 = 2.5 \text{ ms}$$

Voltage across capacitor ; $-[(t-1)/\tau]$


$$V(t) = V(\infty) + [V(1) - V(\infty)] e^{-(t-1)/\tau}$$
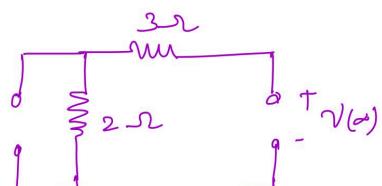
$$V(t) = 0 + (4 - 0) e^{-(t-1)/2.5 \text{ m}} \text{ volt}$$



$$V(t) = 4 e^{-400(t-1)} \text{ Volt}$$
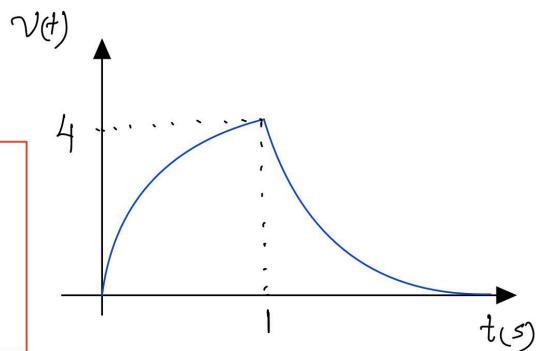
$$V(t) = \begin{cases} 4(1 - e^{-400t}), & 0 < t < 1 \\ 4 e^{-400(t-1)}, & t \geq 1 \end{cases}$$



Soln 3[b]:


Data Given:

$$V_C(0^-) = 2 \text{ V}$$

$$i_L(0^-) = 0 \text{ A}$$

$$V_C(0^+) = V_C(0^-) = V_C(0) = 2 \text{ V}$$
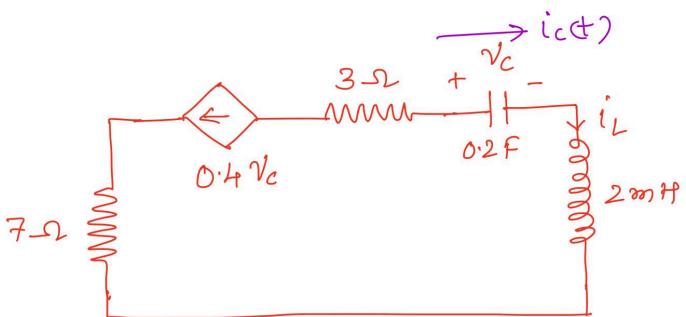
$$i_L(0^+) = i_L(0^-) = i_L(0) = 0 \text{ A}$$



for $t \geq 0$

$$\dot{i}_L(t) = i_c(t) = C \frac{dV_C(t)}{dt} = -0.4 V_C \quad \text{--- (1)}$$

$$0.2 \frac{dV_C(t)}{dt} = -0.4 V_C$$

$$\frac{dV_C(t)}{dt} + 2 V_C(t) = 0$$

$$dV_C(t) = -2 V_C(t) dt$$

$$\int_2 \frac{dV_C(t)}{V_C(t)} = - \int_{t=0}^t 2 dt$$

$$\left[\ln V_C(t) \right]_2^{V_C(t)} = -2 \left[t \right]_0^t = -2t$$

$$\ln \left(\frac{V_C(t)}{2} \right) = -2t$$

$$V_c(t) = 2 e^{-2t}, \quad t > 0$$

from Eqⁿ(1);

$$i_L(t) = C \frac{dV_c(t)}{dt} = 0.2 \times \frac{d}{dt}(2e^{-2t})$$

$$i_L(t) = 0.2 \times 2(-2)e^{-2t}$$

$$i_L(t) = -0.8e^{-2t} \text{ A}, \quad t > 0$$

Soln 4: Data Given:

$$V_s = 36.3 \text{ V}$$

$$R_a = 2 \text{ k}\Omega$$


$$R_b = 3 \text{ k}\Omega$$

$$R_c = 6 \text{ k}\Omega$$

$$C_p = 1 \mu\text{F}$$

$$C_q = 2 \mu\text{F}$$

$$C_r = 3 \mu\text{F}$$

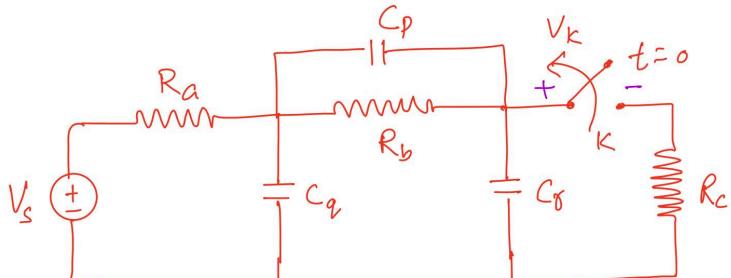

for $t < 0$

$$i = \frac{36.3}{11k} = 3.3 \text{ mA}$$

$$V_{C_p(0^-)} = i \times 3k = 9.9 \text{ V}$$

$$V_{C_r(0^-)} = i \times 6k = 19.8 \text{ V}$$



$$V_{C_q(0^-)} = 36.3 - i \times 2k = 36.3 - 6.6 = 29.7 \text{ V}$$

for $t > 0$

$$V_{C_p(0^+)} = V_{C_p(0^-)} = V_{C_p(0)} = 9.9 \text{ V}$$

$$V_{C_r(0^+)} = V_{C_r(0^-)} = V_{C_r(0)} = 19.8 \text{ V}$$
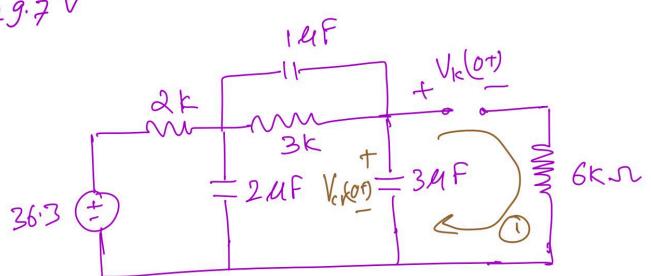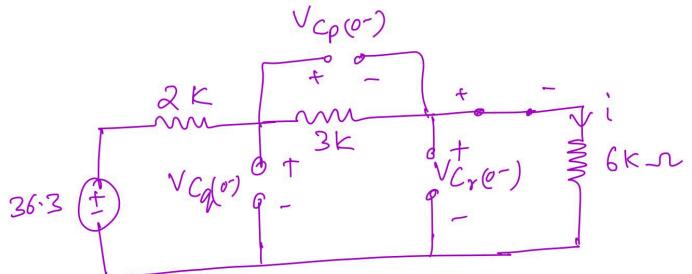
$$V_{C_q(0^+)} = V_{C_q(0^-)} = V_{C_q(0)} = 29.7 \text{ V}$$




Apply KVL in loop ①;

$$-V_K(0^+) + V_{Cr}(0^+) = 0$$

$$\boxed{V_K(0^+) = V_{Cr}(0^+) = 19.8 \text{ V}}$$

Using Nodal Analysis;

KCL at node $V_{Cq}(t)$:

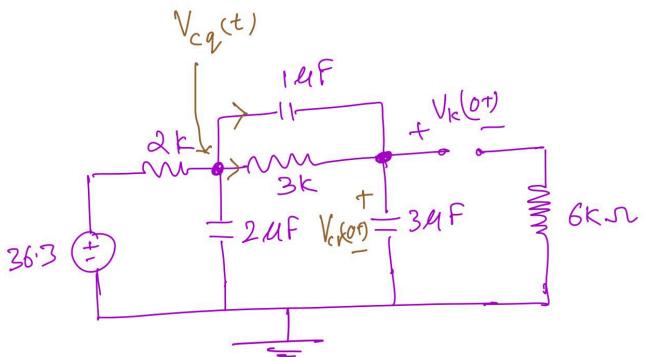

$$\frac{V_{Cq}(t) - 36.3}{2k} + 2u \frac{dV_{Cq}(t)}{dt} + \frac{V_{Cq}(t) - V_K(t)}{3k} + 1u \frac{d[V_{Cq}(t) - V_K(t)]}{dt} = 0$$

$$1u \frac{dV_{Cq}(t)}{dt} + 2u \frac{dV_{Cq}(t)}{dt} = - \left[\frac{V_{Cq}(t) - 36.3}{2k} + \frac{V_{Cq}(t) - V_K(t)}{3k} - 1u \frac{dV_K(t)}{dt} \right]$$

$$\frac{dV_{Cq}(t)}{dt} = -\frac{1}{3u} \left[\frac{V_{Cq}(t) - 36.3}{2k} + \frac{V_{Cq}(t) - V_K(t)}{3k} - 1u \frac{dV_K(t)}{dt} \right] \quad (1)$$

KCL at node $V_K(t)$:

$$1u \frac{d[V_K(t) - V_{Cq}(t)]}{dt} + \frac{V_K(t) - V_{Cq}(t)}{3k} + 2u \frac{dV_K(t)}{dt} = 0$$

$$1u \frac{dV_K(t)}{dt} - 1u \frac{dV_{Cq}(t)}{dt} + \frac{V_K(t) - V_{Cq}(t)}{3k} + 2u \frac{dV_K(t)}{dt} = 0$$

$$1u \frac{dV_K(t)}{dt} + \frac{1}{3} \left[\frac{V_{Cq}(t) - 36.3}{2k} + \frac{V_{Cq}(t) - V_K(t)}{3k} - u \frac{dV_K(t)}{dt} \right] + \frac{V_K(t) - V_{Cq}(t)}{3k} + 3u \frac{dV_K(t)}{dt} = 0$$

$$(4 - \frac{1}{3})u \frac{dV_K(t)}{dt} + \frac{1}{3} \left[\frac{V_{Cq}(t) - 36.3}{2k} + \frac{V_{Cq}(t) - V_K(t)}{3k} \right] + \frac{V_K(t) - V_{Cq}(t)}{3k} = 0$$

at $t=0^+$

$$\frac{11}{3}u \frac{dV_K(0^+)}{dt} + \frac{1}{3} \left[\frac{V_{Cq}(0^+) - 36.3}{2k} + \frac{V_{Cq}(0^+) - V_K(0^+)}{3k} \right] + \frac{V_K(0^+) - V_{Cq}(0^+)}{3k} = 0$$

$$\frac{11}{3}u \frac{dV_K(0^+)}{dt} + \frac{1}{3} \left[\frac{29.7 \cdot 36.3}{2k} + \frac{29.7 - 19.8}{3k} \right] + \frac{19.8 - 29.7}{3k} = 0$$

$$\frac{11}{3} \mu \frac{dV_{lc}(0^+)}{dt} + \frac{1}{3} \left[-\frac{3/2}{R_C} + \frac{3 \cdot 3}{R_K} \right] - \frac{3 \cdot 3}{R_C} = 0$$

$$\frac{dV_{lc}(0^+)}{dt} = \frac{3 \cdot 3 \times 3}{11 R_K \mu} = 900 \text{ V/s}$$

Solⁿ 5:

for $t < 0$



$$i(0^-) = 0 \text{ A}$$

$$V_C(0^-) = \frac{150 \times 5}{30} = 25 \text{ V}$$


for $t > 0$

$$i(0^+) = i(0^-) = i(0) = 0 \text{ A}$$
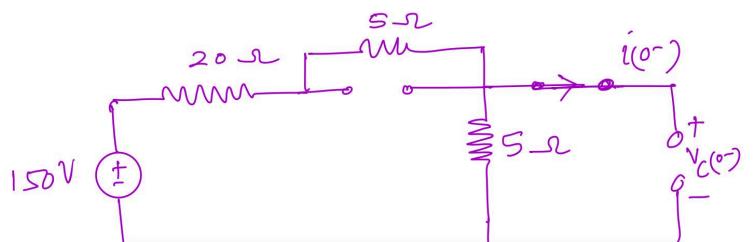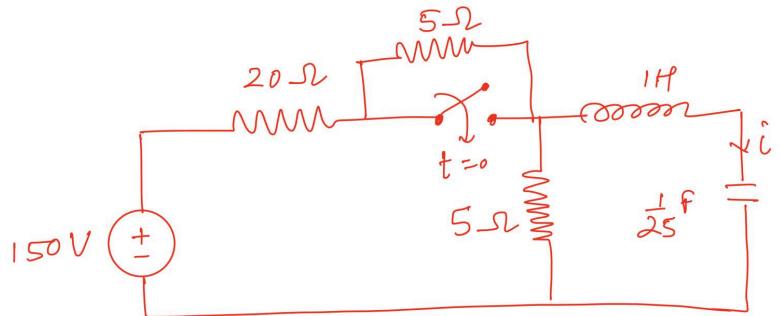
$$V_C(0^+) = V_C(0^-) = V_C(0) = 25 \text{ V}$$




Using source transformation;

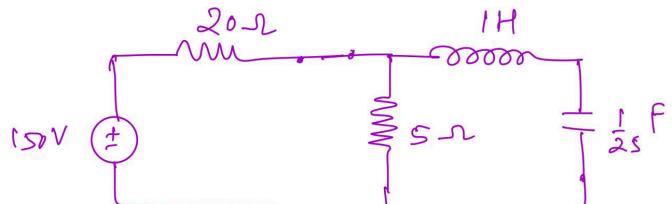

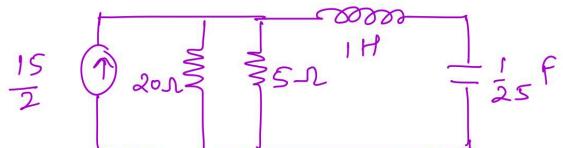a) Apply KVL in loop ①;


$$30 - 4i - 1 \frac{di}{dt} - \frac{1}{25} \int_0^t i dt = 0$$



differentiate w.r.t. t ;

$$0 - 4 \frac{di}{dt} - \frac{d^2i}{dt^2} - 25i = 0$$
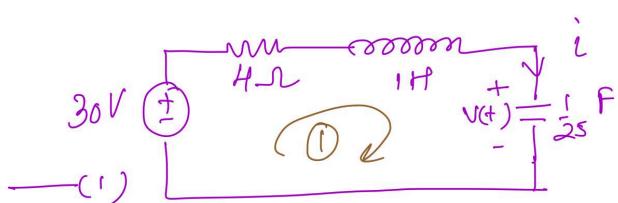
$$\frac{d^2i}{dt^2} + 4 \frac{di}{dt} + 25i = 0$$



Eqn (1) is the 2nd order differential equation.

Substitute $i = ke^{st}$

$$k s^2 e^{st} + 4kse^{st} + 25ke^{st} = 0$$

$$ke^{st} (s^2 + 4s + 25) = 0$$

$$s^2 + 4s + 25 = 0 \quad \text{characteristics equation}$$

b) roots of characteristics equation;

$$s_{1,2} = \frac{-4 \pm \sqrt{16 - 100}}{2 \times 1}$$

$$s_{1,2} = -2 \pm j4.583$$

$$s_1 = -2 + j4.583 \quad \text{roots of characteristics eqn}$$

$$s_2 = -2 - j4.583 \quad \alpha = 2, \omega = 4.583$$

\therefore roots are complex conjugate.

\therefore response is underdamped in nature.

c) $V(t) = V_{ss}(t) + V_{tr}(t)$

$$V_{ss}(t) = V(t)|_{t \rightarrow \infty} = 30V$$

$$V_{tr}(t) = e^{-at} [A \cos \omega t + B \sin \omega t]$$

$$V(t) = 30 + e^{-2t} [A \cos 4.583t + B \sin 4.583t] \quad (1)$$

$$\text{at } t=0, V(0) = 25V$$

$$V(0) = 30 + e^{-2 \times 0} [A \cos 0 + B \sin 0] = 25$$

$$A = -5$$

$$\text{at } t=0, i(0) = 0$$

$$i(t) = C \frac{dV(t)}{dt}$$

$$0 = i(0) = \frac{1}{25} \left[e^{-2t} (-4.583A \sin 4.583t + 4.583B \cos 4.583t) \right. \\ \left. + (A \cos 4.583t + B \sin 4.583t) \times (-2e^{-2t}) \right] \text{ at } t=0$$

$$0 = e^0 [0 + 4.583B + (A + 0)(-2)e^0]$$

$$0 = 4.583B - 2A$$

$$B = \frac{2A}{4.583} = \frac{2 \times (-5)}{4.583} = 2.182 \quad , \quad \boxed{B = 2.182}$$


From eqn(1),

$$V(t) = 30 + e^{-2t} [-5 \cos 4.583t + 2.182 \sin 4.583t]$$

$$i(t) = C \frac{dV(t)}{dt} = \frac{1}{25} \left[e^{-2t} (-5 \times 4.583 \sin 4.583t + 2.182 \times 4.583 \cos 4.583t) \right. \\ \left. + (-5 \cos 4.583t + 2.182 \sin 4.583t) (-2e^{-2t}) \right]$$


$$i(t) = \frac{1}{25} e^{-2t} \left[-22.91 \sin 4.583t + 10 \cos 4.583t + 10 \cos 4.583t \right. \\ \left. - 4.364 \sin 4.583t \right]$$
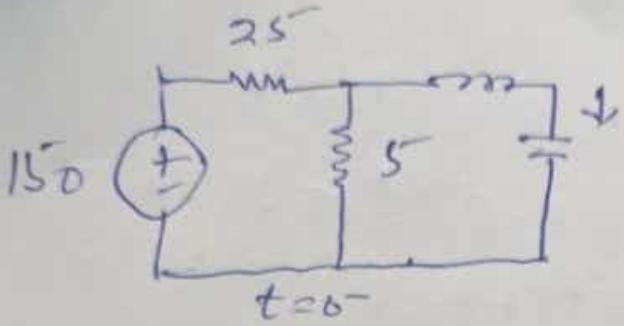
$$\boxed{i(t) = \frac{1}{25} \left[-27.27 \sin 4.583t + 20 \cos 4.583t \right] e^{-2t} A}$$







$$\frac{25 \times 5}{30} = \frac{25}{6}$$

$$\frac{20 \times 4}{30} = 4$$

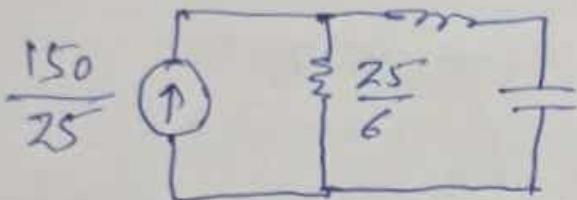


$t > 0$

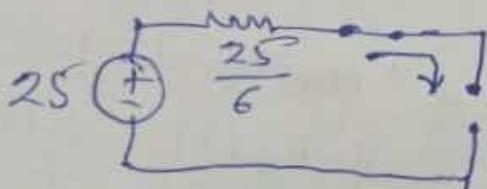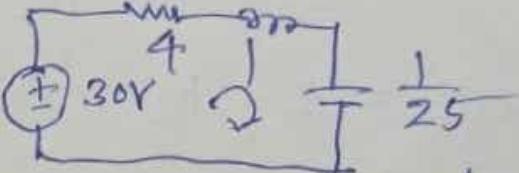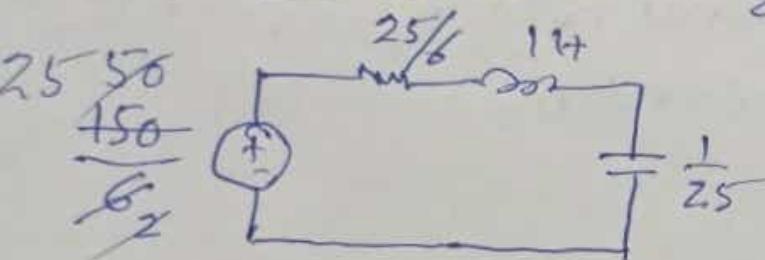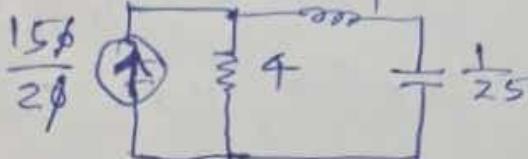

$$i(0^+) = i(0^-) = 0$$

$$v_c(0^+) = v_c(0^-) = 25$$

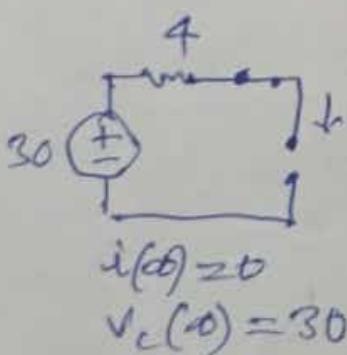

$$4i + \frac{di}{dt} + 25 \int_{-\infty}^t i \, dt = 30$$

$$4i + \frac{di}{dt} + 25 \int_{-\infty}^0 i \, dt + 25 \int_0^t i \, dt = 30$$

$$\frac{di}{dt} + 4i + 25 + 25 \int_0^t i \, dt = 30$$

$$\frac{di}{dt} + 4i + 25 \int_0^t i \, dt = 5$$

$$\therefore \frac{di(0^+)}{dt} + 4i(0^+) = 5$$

$$\frac{di(0^+)}{dt} = 5$$

$$\frac{d^2i}{dt^2} + 4 \frac{di}{dt} + 25i = 0$$

$$\delta^2 + 4\delta + 25 = 0$$

$$\delta_1, \delta_2 = -4 \pm \sqrt{16 - 4 \times 25} \over 2$$

$$\delta_1, \delta_2 = -2 \pm \frac{\sqrt{-21}}{2} = -2 \pm \frac{1}{2}\sqrt{21}$$

$$\begin{aligned}
 i(t) &= A_1 e^{-2t} + A_2 e^{j\sqrt{21}t} \\
 &= A_1 e^{(-2+j\sqrt{21})t} + A_2 e^{(-2-j\sqrt{21})t} \\
 &= A_1 e^{-2t} \cdot e^{j\sqrt{21}t} + A_2 e^{-2t} \cdot e^{-j\sqrt{21}t} \\
 &= e^{-2t} \left\{ A_1 e^{j\sqrt{21}t} + A_2 e^{-j\sqrt{21}t} \right\} \\
 &= e^{-2t} \left\{ A_1 (\cos\sqrt{21}t + j \sin\sqrt{21}t) \right. \\
 &\quad \left. + A_2 (\cos\sqrt{21}t - j \sin\sqrt{21}t) \right\} \\
 &= e^{-2t} \left\{ (A_1 + A_2) \cos\sqrt{21}t + j(A_1 - A_2) \sin\sqrt{21}t \right\} \\
 &= e^{-2t} \left\{ A_3 \cos\sqrt{21}t + A_4 \sin\sqrt{21}t \right\}
 \end{aligned}$$

$$0 = i(0^+) = 1 \left\{ A_3 + 0 \right\}$$

$$A_3 = 0$$

$$\begin{aligned}
 \frac{di(t)}{dt} &= (-2) e^{-2t} \left\{ A_3 \cos\sqrt{21}t + A_4 \sin\sqrt{21}t \right\} \\
 &\quad + e^{-2t} \left\{ -A_3 \sqrt{21} \sin\sqrt{21}t + A_4 \sqrt{21} \cos\sqrt{21}t \right\}
 \end{aligned}$$

$$S = \frac{di(t)}{dt} = (-2) \left\{ A_3 + 0 \right\} + 0 \left\{ 0 + A_4 \sqrt{21} \right\}$$

$$S = -2A_3 + A_4 \sqrt{21}$$

$$A_4 = \frac{S}{\sqrt{21}}$$

$$\boxed{\therefore i(t) = e^{-2t} \times \frac{S}{\sqrt{21}} \sin\sqrt{21}t}$$

Applying Laplace.

$$\left\{ 8I(s) - i(0^+) \right\} + 4I(s) + 25 \frac{I(s)}{s} = \frac{S}{s}$$

$$8I(s) + 4I(s) + 25 \frac{I(s)}{s} = \frac{S}{s}$$

$$\frac{\{8s^2 + 4s + 25\} I(s)}{s} = \frac{S}{s}$$

$$F(s) = \frac{s}{(s^2 + 4s + 25)} = \frac{s}{s^2 + 4s + 4 + 21}$$

$$F(s) = \frac{s - \sqrt{21}}{\sqrt{21} \{ (s+2)^2 + (\sqrt{21})^2 \}}$$

$$x(t) = \frac{s}{\sqrt{21}} e^{-2t} \sin \sqrt{21} t.$$